



### Amp Selector Amp Diagram

- Relay number corresponds to Arduino pin number
- Common on all goes to Guitar In
- Normally Closed is always empty
- Normally Open goes to Out Jack
- 5 Out Jacks - 1 for each Amp
- R4-7 on Seeed Relay v2.1 - no use here
- R8 Single Relay set to High Trigger